
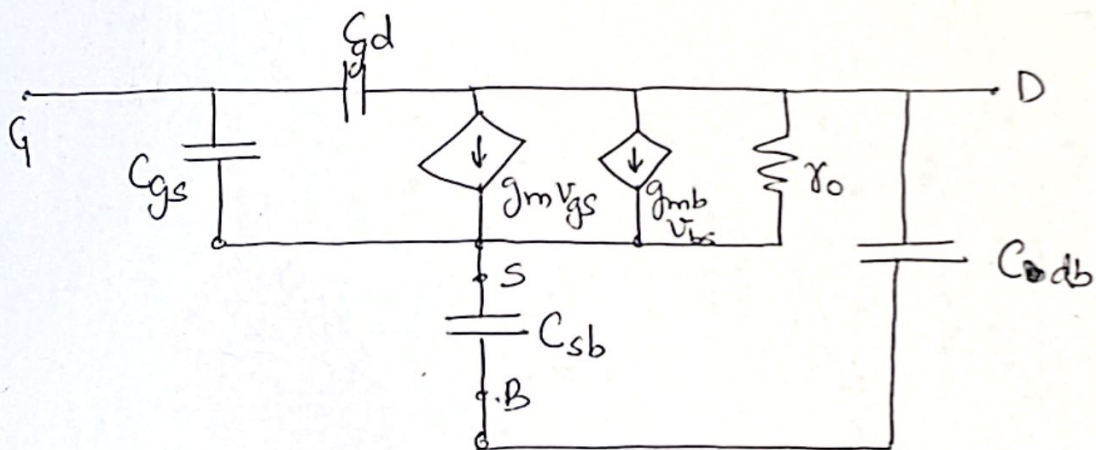
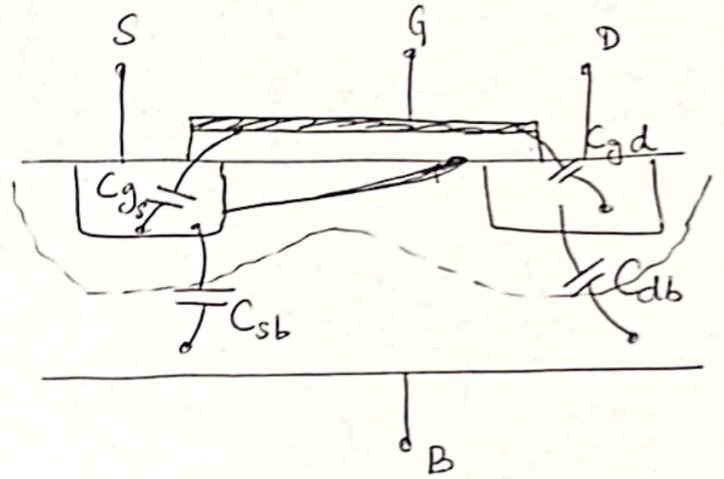


# Lec 21: Frequency Response of Amplifiers

## Review

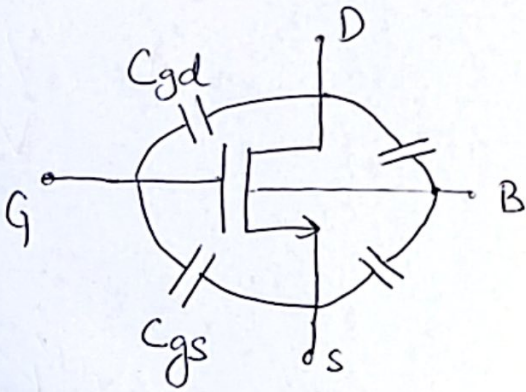

$$C_{gs} = WL_{ov} C_{ox} + \frac{2}{3} WL C_{ox}$$

$$C_{gd} = WL_{ov} C_{ox}$$

$$C_{sb} = \frac{C_{sb0}}{\left(1 + \frac{V_{sb}}{\psi_0}\right)^{1/2}}$$

$$C_{db} = \frac{C_{db0}}{\left(1 + \frac{V_{db}}{\psi_0}\right)^{1/2}}$$


Typically:  $C_{gs} > C_{gd} > C_{sb} > C_{db}$ .

# Miller Effect \* Miller's Theorem


Thm: If circuit (1) can be converted to circuit (2),

$$\text{then } Z_1 = \frac{Z}{1-A_v} \quad \& \quad Z_2 = \frac{Z}{1-A_v^{-1}} \quad \text{where } A_v = \frac{V_y}{V_x}$$

Circuit (1)

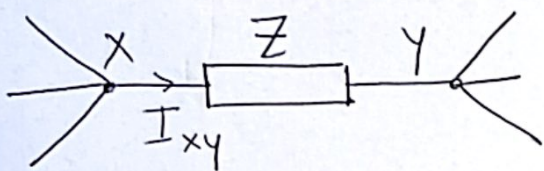

Circuit (2)

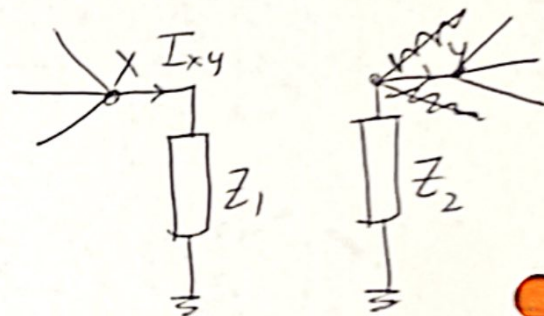


Proof

$$I_{xy} = \frac{V_x - V_y}{Z} = \frac{V_x}{Z_1} = -\frac{V_y}{Z_2}$$

$$\Rightarrow Z_1 = \frac{Z}{1 - \frac{V_y}{V_x}} \quad \& \quad Z_2 = \frac{Z}{1 - \frac{V_x}{V_y}}$$


Caution: Note the if condition

# Miller Effect

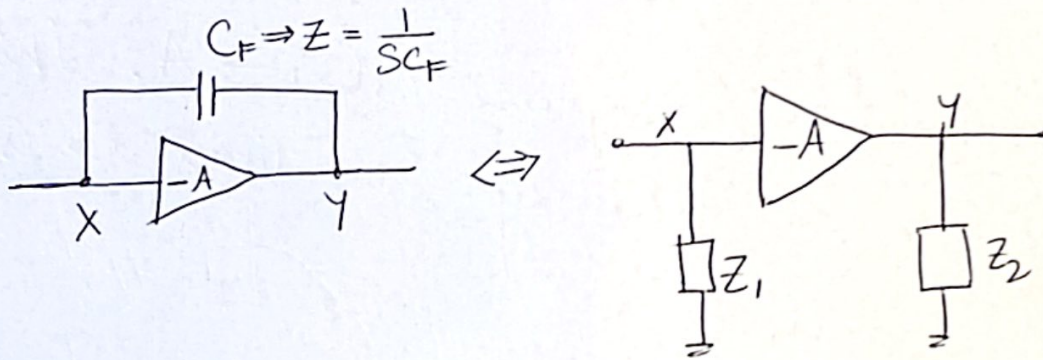


$$Z = \frac{1}{sC_F} \Rightarrow Z_1 = \frac{1/sC_F}{1+A} ; Z_2 = \frac{1/sC_F}{1+A^{-1}}$$
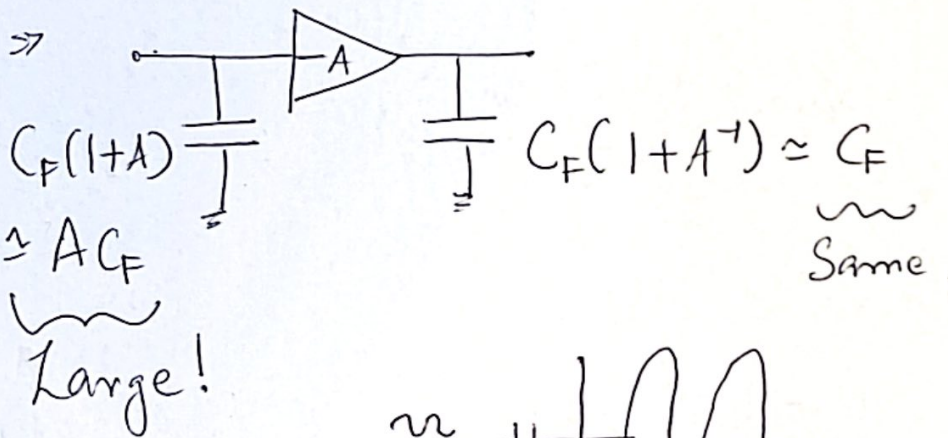
$$Z_1 = \frac{1}{s(C_F(1+A))} ; Z_2 = \frac{1}{s(C_F(1+A^{-1}))}$$




## Intuition

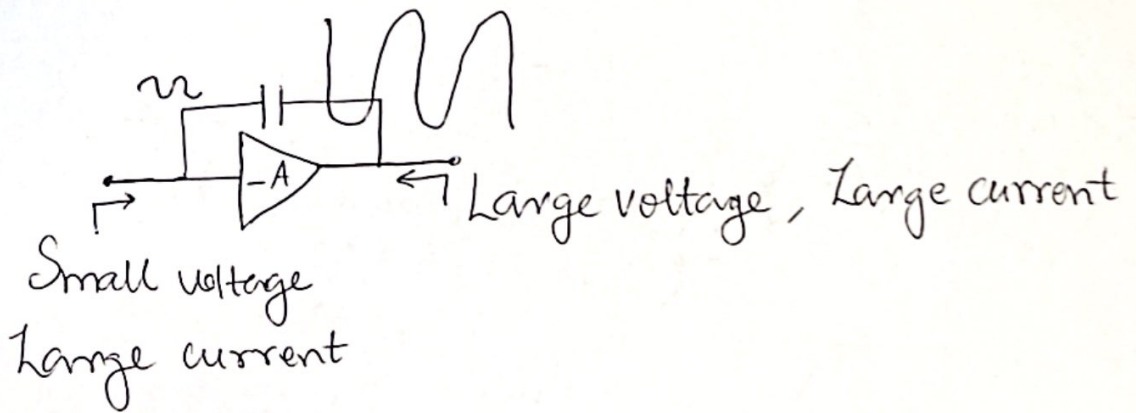

Note: Here  $A$  should really be  $AC(s)$  & include the

effect of the capacitor as well!

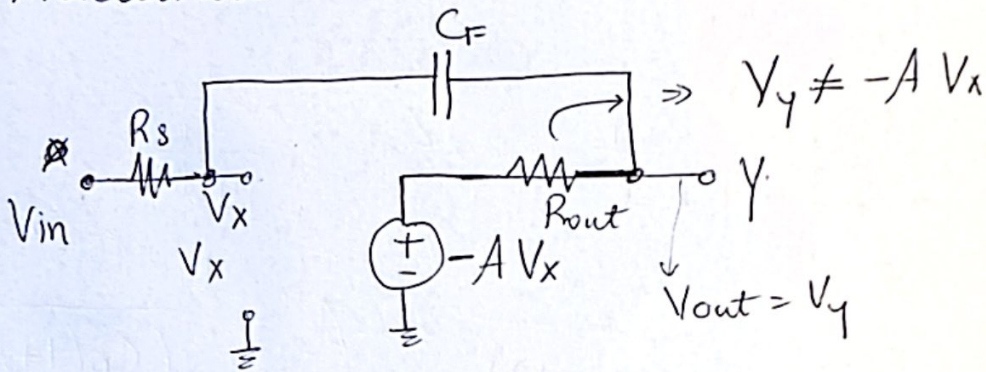Miller Approximation: Replace  $A(s) \rightarrow A$ . This needs to be done carefully. Sometimes leads to inaccurate results.




$$\frac{V_{in} - V_x}{R_s} R_{out} = V_{out} + A V_x$$

$$\frac{V_{in} - V_x}{R_s} = (V_x - V_{out}) s C_F$$


Solving  $\Rightarrow \frac{V_{out}}{V_{in}} = \frac{R_{out} s C_F - A}{[(A+1)R_s + R_{out}] C_F s + 1}$

$$\omega_z = \frac{A}{R_{out} C_F}$$
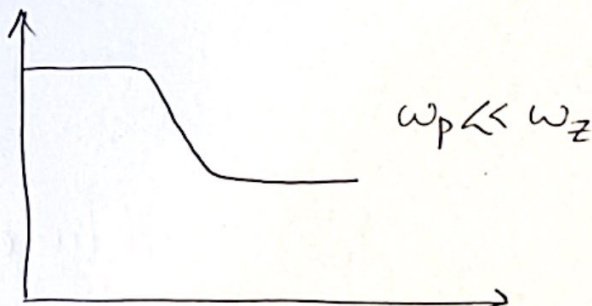
$$\omega_p = \frac{-1}{(A+1)R_s C_F + R_{out} C_F}$$



Miller  $\Rightarrow$

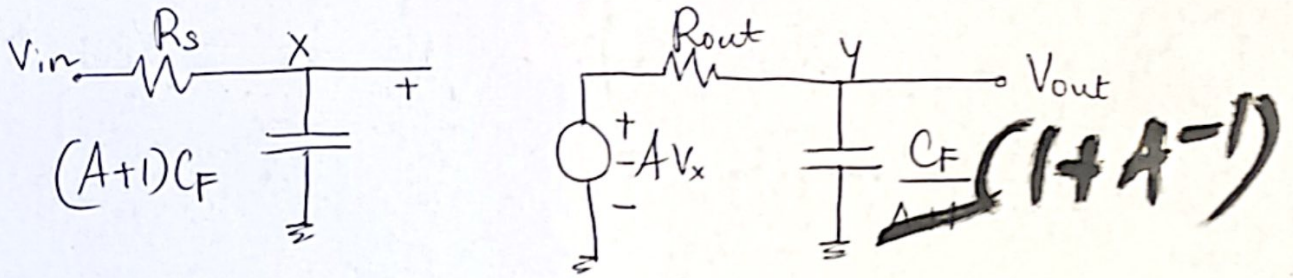

$$\text{Solving } \Rightarrow \frac{V_{out}}{V_{in}} = \frac{-A}{[(1+A)R_s C_F s + 1] \left( \frac{1}{1+A} C_F R_{out} s + 1 \right)}$$


$\Rightarrow$  No zero & 2 poles!

$$\omega_{p1} = \frac{-1}{(1+A)R_s C_F}, \quad \omega_{p2} = \frac{-1}{\frac{1}{1+A} C_F R_{out}}$$

### Limitations of Miller Approximation


- 1) Eliminate zeroes
  - 2) Add poles
  - 3) Inaccurate output impedance.
- > Good for intuition/simplification & input impedance  
or input cap boost!
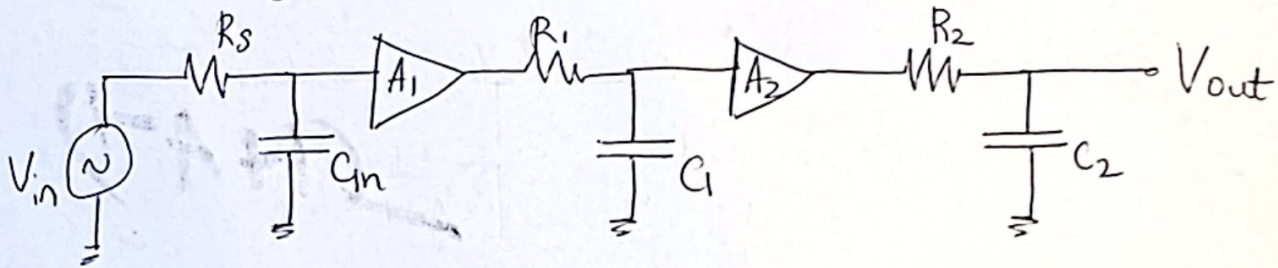
## Associating Poles with Nodes (Approximate method).



$$\frac{V_{out}}{V_{in}} = \frac{A_1}{1 + R_s C_{in} s} \cdot \frac{A_2}{1 + R_1 C_1 s} \cdot \frac{1}{1 + R_2 C_2 s}$$

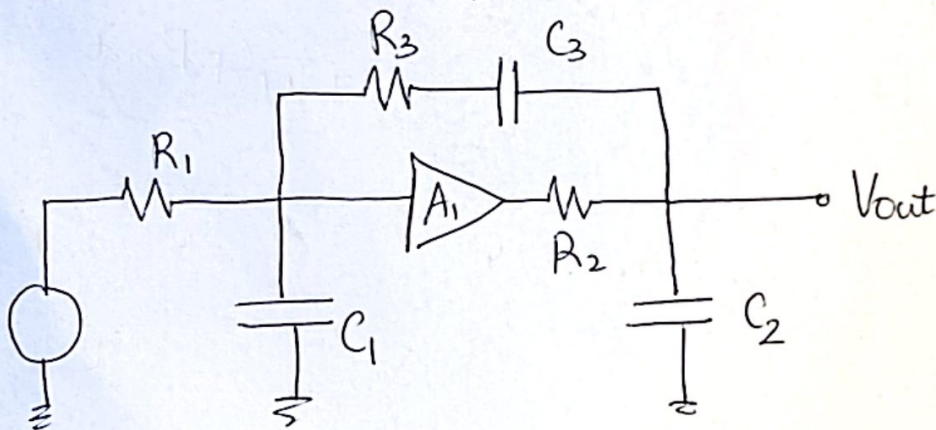
- > Each node with RC contributes 1 pole.
- > This heuristic approach will be made rigorous later.




→ How can we treat this?  
Miller!

- > This can be converted to 2 pole case & treated but must be careful!
- > Note: This method is valid under a "dominant pole approximation" → will derive rigorously later.

# Common Source

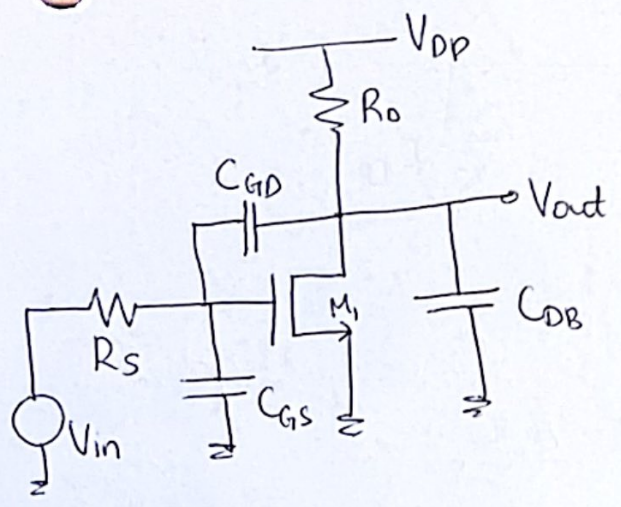

= Miller

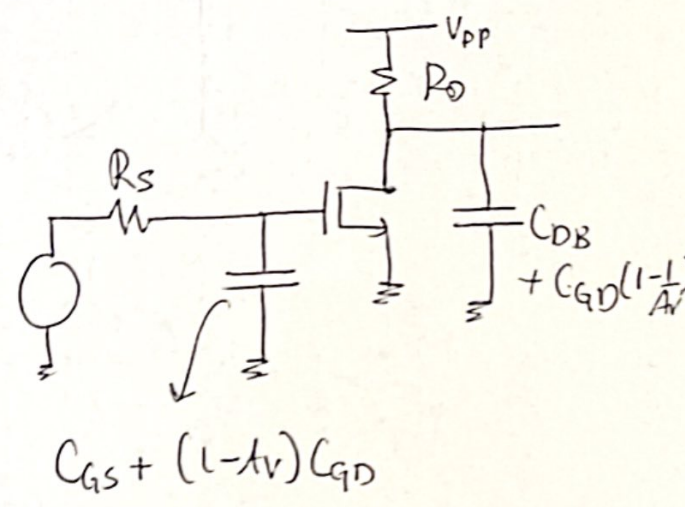


$$\omega_{in} = \frac{1}{R_s (C_{GS} + (1 + g_m R_o) C_{GD})}$$

$$\omega_{out} \approx \frac{1}{R_o (C_{DB} + C_{GD})}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_m R_o}{\left(1 + \frac{s}{\omega_{in}}\right) \left(1 + \frac{s}{\omega_{out}}\right)}$$

## Direct (Brute Force)

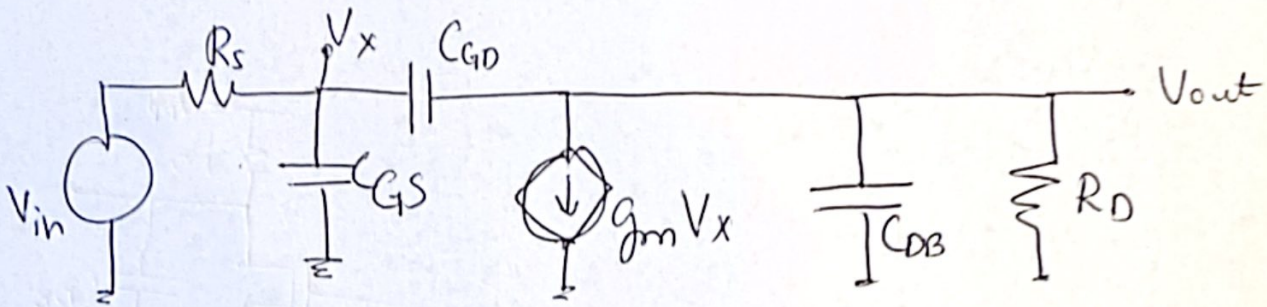

$$\frac{V_x - V_{in}}{R_s} + \frac{V_x}{\frac{1}{sC_{gs}}} + \frac{(V_x - V_{out})}{\frac{1}{sC_{gd}}} = 0$$

$$(V_{out} - V_x) s C_{gd} + g_m V_x + V_{out} \left( \frac{1}{R_D} + s C_{db} \right) = 0$$

Solving,

$$\frac{V_{out}}{V_{in}} = \frac{(sC_{gd} - g_m) R_D}{R_s R_D (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db}) s^2}$$

$$+ \left[ R_s (1 + g_m R_D) C_{gd} + R_s C_{gs} + R_D (C_{gd} + C_{db}) \right] s + 1$$

$$D(s) = \left( \frac{s}{\omega_{p1}} + 1 \right) \left( \frac{s}{\omega_{p2}} + 1 \right) = \frac{s^2}{\omega_{p1} \omega_{p2}} + \left( \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} \right) s + 1$$

If  $|\omega_{p1}| \ll |\omega_{p2}|$ , coeff of  $s$  is  $\approx \frac{1}{\omega_{p1}}$

$$\Rightarrow \omega_{p1} \approx \frac{1}{R_s (1+g_m R_D) C_{gd} + R_s C_{gs} + \underbrace{R_D (C_{gd} + C_{db})}_{\text{missing term}}}$$

Recall,

$$\omega_{in} \approx \frac{1}{R_s (1+g_m R_D) C_{gd} + R_s C_{gs}}$$

↓  
missing term.

Coeff of  $S^2 = (\omega_{p1} \omega_{p2})^{-1}$


$$\Rightarrow \omega_{p2} = \frac{1}{\omega_{p1}} \cdot R_s R_D (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db})$$

$$= \frac{R_s (1+g_m R_D) C_{gd} + R_s C_{gs} + R_D (C_{gd} + C_{db})}{R_s R_D (C_{gs} C_{gd} + C_{gs} C_{db} + C_{gd} C_{db})}$$

If  $C_{gs} \gg (1+g_m R_D) C_{gd} + R_D (C_{gd} + C_{db}) / R_s$

$$\Rightarrow \omega_{p2} \approx \frac{R_s C_{gs}}{R_s R_D (C_{gs} C_{gd} + C_{gs} C_{db})}$$

$$= \frac{1}{R_D (C_{gd} + C_{db})}$$

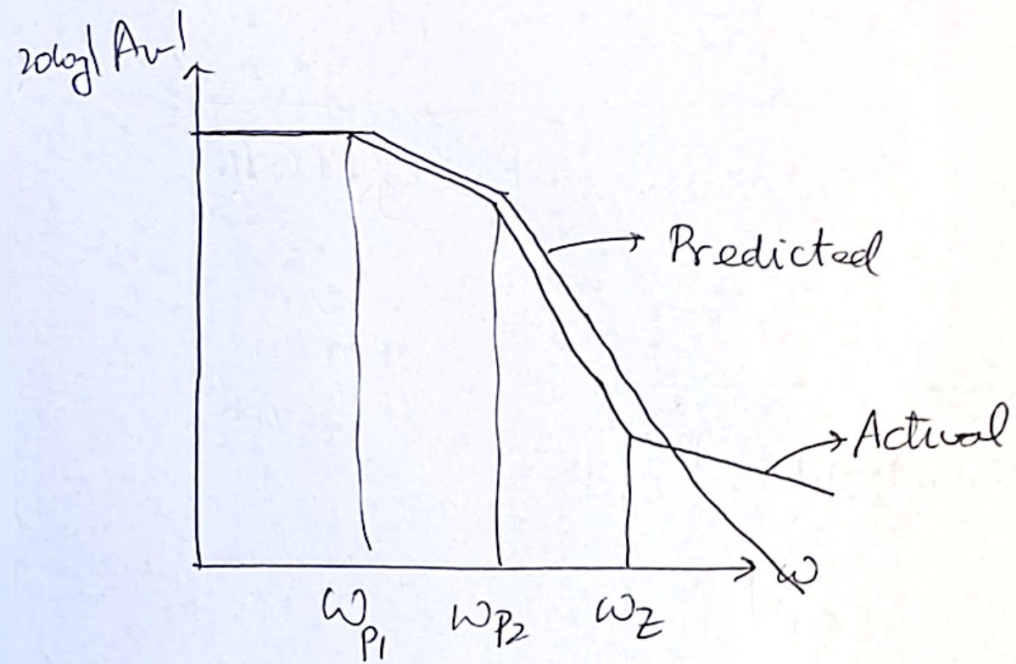

If  $C_{gs}$  dominates  $C_{gd}$  &  $C_{db}$ , the approximation is OK